IOT Assignment

P.Sravan kumar sravankumar912126@gmail.com IITH - Future Wireless Communications-(FWC22043)

Contents

1	Introduction	1
2	Method to solve	1
3	Components	1
4	Distributive law proof with truth table	1
5	Connections	1
6	Conclusion	1

Α $\overline{\mathsf{c}}$ x(LHS) y(RHS) 0 0 0 1 0 0 0 0 0 1 0 0 1 1 0 0 0 0 0 0 1 1 1 1 1 0 1 1 1 1 1 1

Table 2:

1 Introduction

There are different type of boolean algebra rules to simplify the boolean expression. One of the important law is distributive law. This can be stated as follows: A.(B+C)=A.B+A.C (OR distributive law). A+(B.C)=(A+B).(A+C) (AND distributive law).

5 Connections

Make connections to the LED's and Vamanboard based on table3 and figure1.

Vaman Pins	4	5	7	GND
LED	LED1+	LED2+	LED3+	-ve of 3 LED's

Table 3:

2 Method to solve

To prove distributive law I used 3 IED's for LHS(A.(B+C)), RHS((A+B).(A+C)) and for condition of LHS=RHS.

6 Conclusion

The output of LED3 is 1 for all possible inputs. So LHS=RHS i.e A.(B+C)=A.B+A.C hence distributive law verified.

code link:

 ${\it https://github.com/Sravan24365/iith-fwc/tree/main/iot}$

3 Components

Component	value	quantity
Resistor	220 ohm	1
Arduino	UNO	1
LED		3
Bread board		1
Jumper wires	M-M	20

Table 1:

4 Distributive law proof with truth table