

# Distributive law proof using Arduino

P.Sravan kumar

sravankumar912126@gmail.com

IITH - Future Wireless Communications-(FWC22043)

## Contents

1	Introduction	1
2	Method to solve	1
3	Components	1
4	Distributive law proof with truth table	1
5	Connections	1
6	Conclusion	1

## 1 Introduction

There are different type of boolean algebra rules to simplify the boolean expression. One of the important law is distributive law. This can be stated as follows:  $A.(B+C)=A.B+A.C$  (OR distributive law).  $A+(B.C)=(A+B).(A+C)$  (AND distributive law).

## 2 Method to solve

To prove distributive law I used seven segment display and 7447 IC to control it using binary. Take 3 variables a,b,c and take another 2 variables x,y for LHS ( $A.(B + C)$ ) and RHS ( $A.B + A.C$ ).

If they are equal the seven segment display display's 1 else display's 0. By changing three boolean variables we can observe the distributive law satisfies or not for different inputs. Like these we can prove the distributive law.

code link :

<https://github.com/Sravan24365/iith-fwc/blob/main/assign1%20ide/codes/src/main.cpp>

## 3 Components

Component	value	quantity
Resistor	220 ohm	1
Arduino	UNO	1
sevensegment display		1
decoder	7447	1
Bread board		1
Jumper wires	M-M	20

Table 1:

## 4 Distributive law proof with truth table

A	B	C	x(LHS)	y(RHS)
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Table 2:

## 5 Connections

Make connections to the Sevensegment display and 7447 IC based on table 3 and figure 1.

7447	a'	b'	c'	d'	e'	f'	g'
Display	a	b	c	d	e	f	g

Table 3:

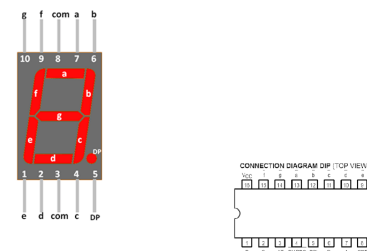


Figure 1:Sevensegment and 7447 IC.

Also make connections to arduino UNO ,7447 IC and inputs based on below table

Arduino UNO	2	3	4	5	6	7	8
7447	A	B	C	D			
input					k	l	m

## 6 Conclusion

The output of sevenseg is 1 for all possible inputs. So  $x=y$  i.e.  $A.(B+C)=A.B+A.C$  hence distributive law verified.